

# LAB Experiment 9

## Boolean Function using Universal Gates

S.V.Harshith EE19BTECH11018


November 20,2020

### 1 Aim

Implement the below logic function in NgSpice using NOR gates using subcircuits.


Input1	Input 2	Output1	Output2
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

### 2 Procedure

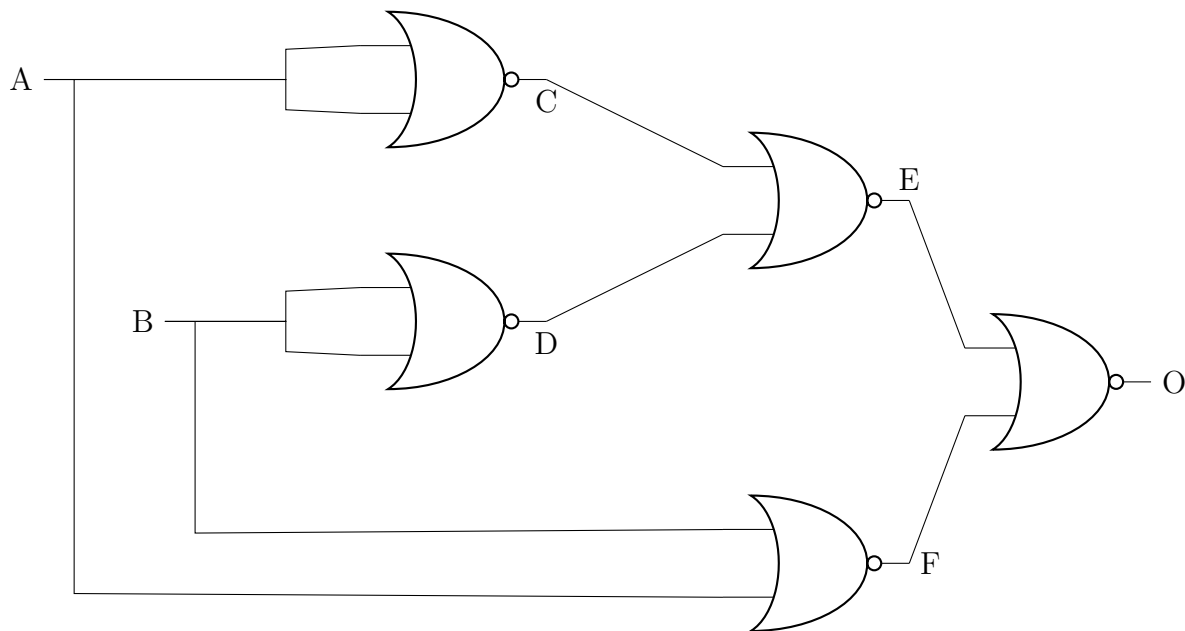

Write the script for the above circuit in NgSpica and plot nodes A,B,O,E as  $V_{in1}$ ,  $V_{in2}$ ,  $V_{out1}$ ,  $V_{out2}$  respectively

### 3 Results

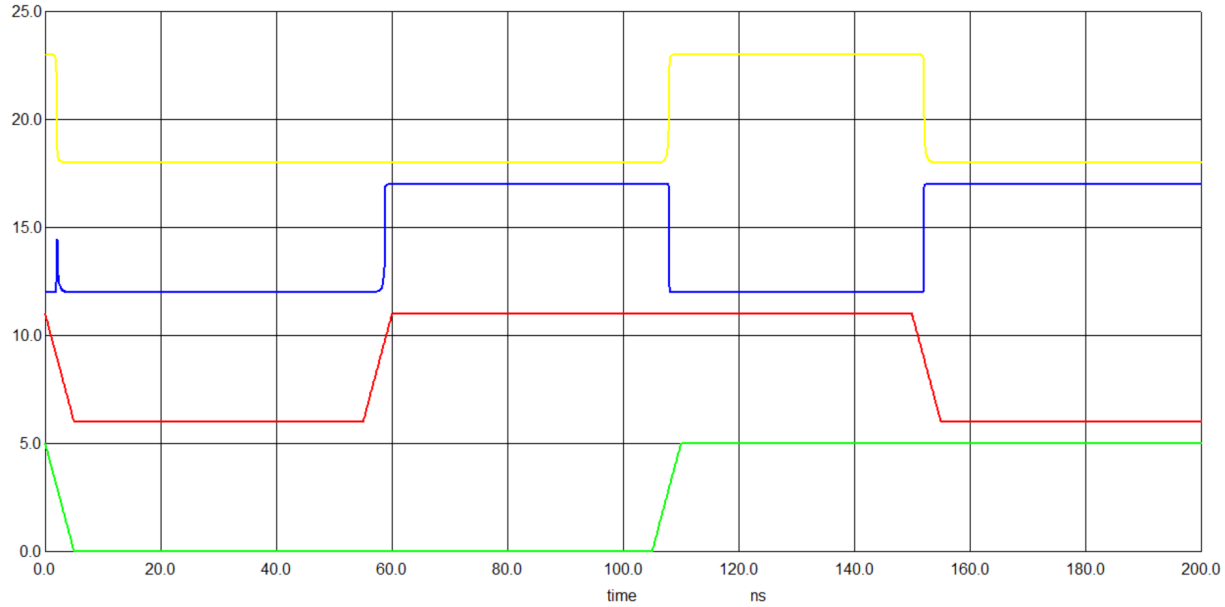

### 4 Understanding

From the circuit diagram we can see that -

- $C = \overline{A + A} = \overline{A}$  and  $D = \overline{B + B} = \overline{B}$
- So  $E = \overline{\overline{A} + \overline{B}} = A.B = \text{AND}(A,B)$
- $O = \overline{E + F} = \overline{A.B + \overline{A + B}} = \overline{A.B + \overline{A + B}} = \overline{A.B}.\overline{\overline{A + B}} = A.\overline{B} + \overline{A}.B = (\overline{A} + \overline{B}).(A + B) = \text{XOR}(A,B)$

And we can check that the above plot follows the below truth table

$A = V_{in1}(Green)$	$B, V_{in2}(Red)$	$O, V_{out1}(Blue)$	$E, V_{out2}(Yellow)$
0	0	0	0
0	1	1	0
1	1	0	1
1	0	1	0

### 5 Conclusion

We can see that Output1 corresponds to a XOR gate and Output2 to AND gate.

Both of these gates can be combined to construct a half adder circuit which is used to add two binary digits.

XOR gate gives the sum and AND gate gives the carry.